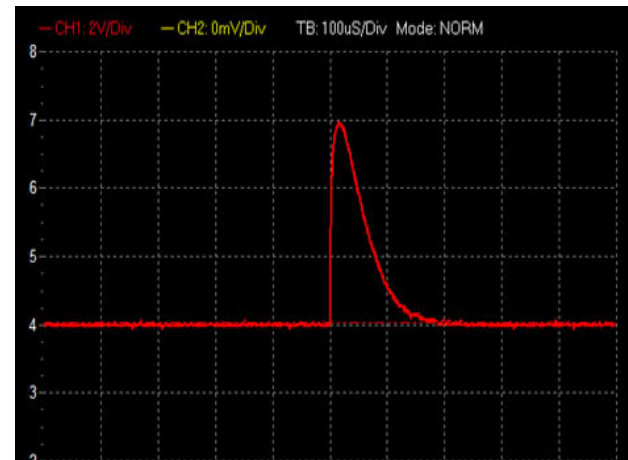


ELECTRONICS - 2b



Pulse-processing units: “rude” role classification

Basic operation

- Preamplifier
- Linear/fast amplifier
- Discriminator
- Time pick-off
- etc

“Assistance”




- Splitter (f-in/f-out)
- Delay

“Permission”

- Linear gate
- Coincidence
- And

Result

- Counter
- TAC
- MCA/ADC
- ...

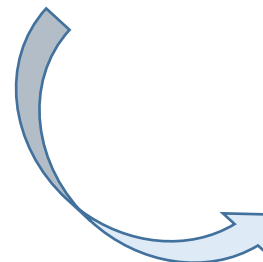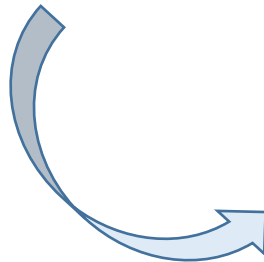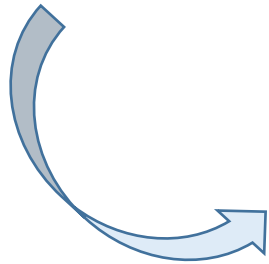

Results: Time-to-amplitude converter (TAC)

- The distribution of the time intervals between start and stop pulses



566 Time-to-Amplitude Converter

- For time spectroscopy in the range from 10 ns to 2 ms
- Valid Start and Valid Conversion outputs
- Selectable output delay and width
- Output synchronized with a stop or external strobe signal
- Provision to reject unwanted start input signals
- Positive or negative input signals


The ORTEC Model 566 Time-to-Amplitude Converter (TAC) measures the time interval between pulses to its start and stop inputs and generates an analog output pulse proportional to the measured time. Timing experiments requiring time ranges from 10 ns to 2 ms may be performed, giving the experimenter flexibility in analyzing random nuclear events that occur within a selected time range. Time ranges from 50 ns to 2 ms are provided via the front-panel controls.

Results: Time-to-amplitude converter (TAC)


(multichannel spectroscopy)

Recording time spectrum

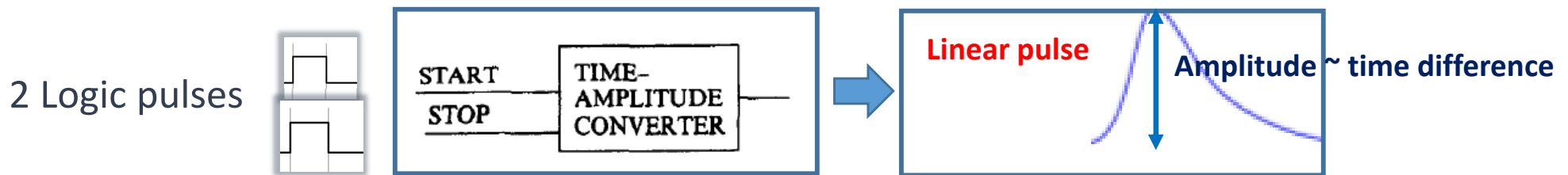- The distribution of time intervals between start and stop pulses (= output pulses of TAC)



- In practice:

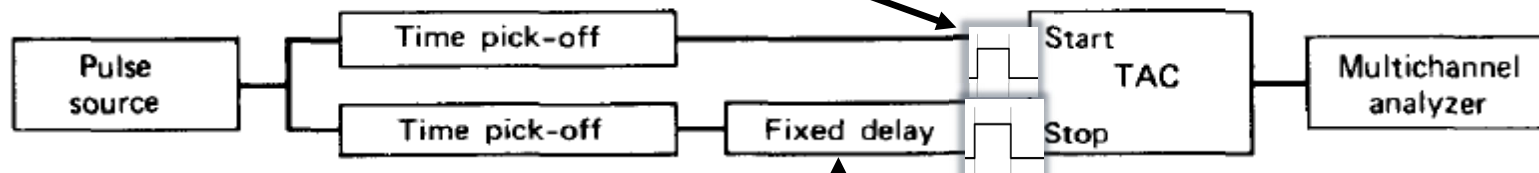

to avoid that half of the pulse would not be visible when it appears at the zero-value of the pulse height axis in the MCA (as is the case for pulses that are coincident)

Results: Multi-channel analyzer (MCA)

Pulse-height analysis system

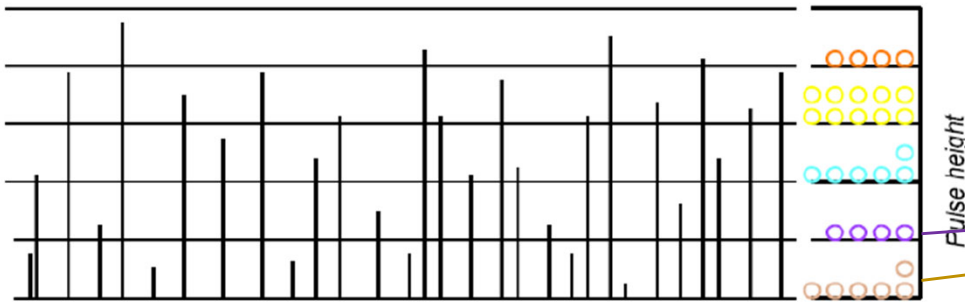


Figure 21: Train of pulses delivered at the output detector

events with the same pulse height (energy, time diff.) in a single channel *(multichannel spectroscopy)*

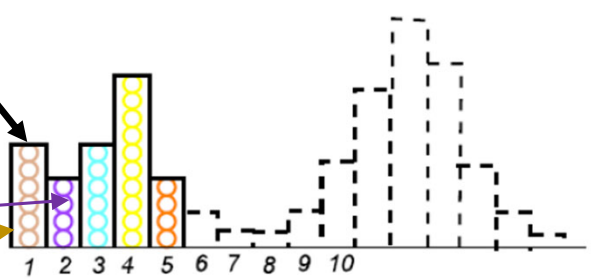


Figure 22 Pulse height spectrum

Results: Analog-to-Digital Converter (ADC)

Pulse-height analysis system

(multichannel spectroscopy)

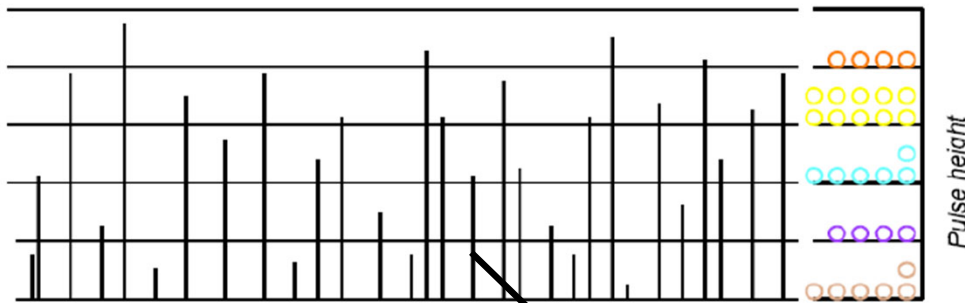


Figure 21: Train of pulses delivered at the output detector

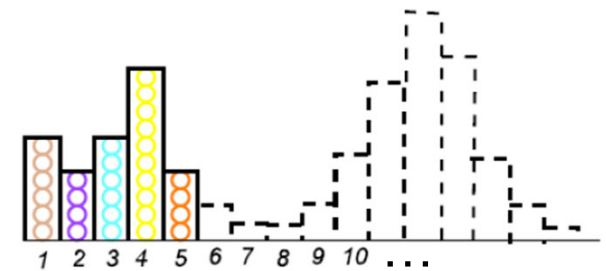


Figure 22: Pulse height spectrum

Analog-to Digital Converter (ADC)


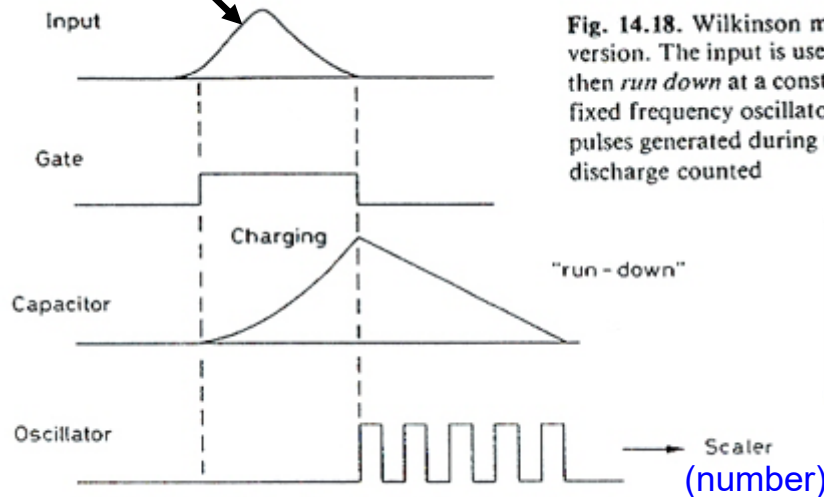


Fig. 14.18. Wilkinson method of analog-to-digital conversion. The input is used to charge a capacitor which is then run down at a constant current. At the same time, a fixed frequency oscillator is gated on and the number of pulses generated during the time it takes the capacitor to discharge counted

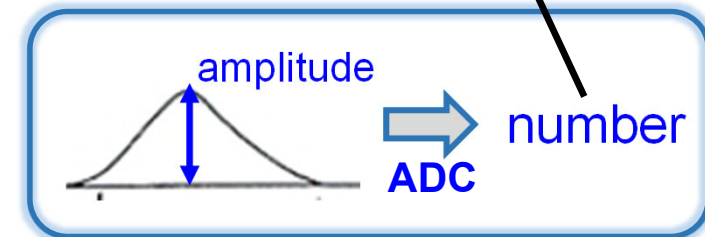

- The ADC converts analog info from the pulse train into digital format
- Registered number is proportional to pulse height

Results: Multi-channel analyzer (MCA)

Pulse-height analysis system

(multichannel spectroscopy)

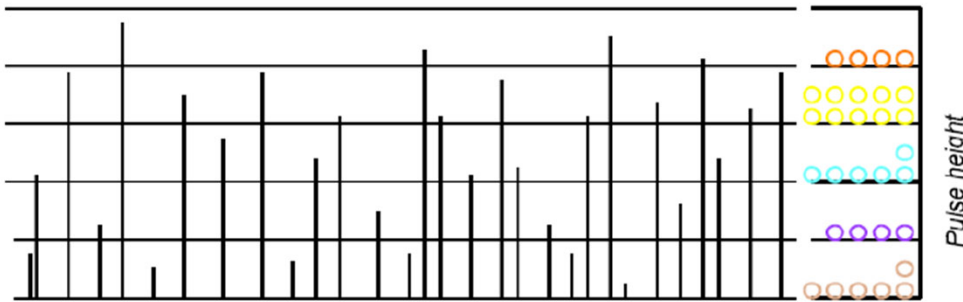


Figure 21: Train of pulses delivered at the output detector



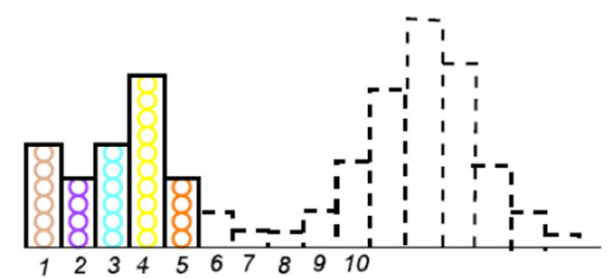
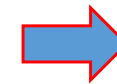
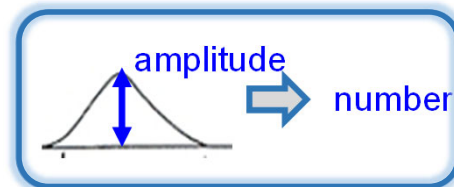
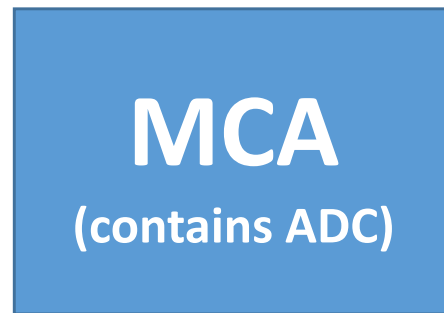
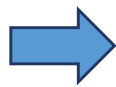


Figure 22 Pulse height spectrum

Linear pulse

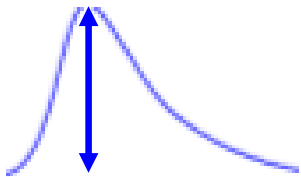

SPECTRUM

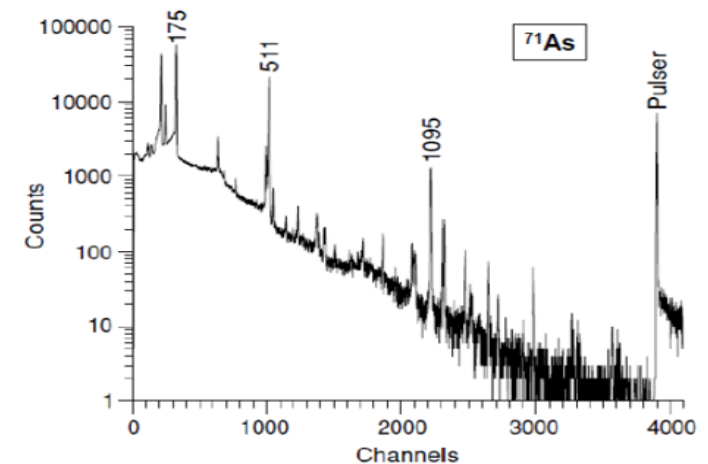


(©Canberra)

Results: Time-to-amplitude converter (TAC) - bis


(multichannel spectroscopy)

Recording time spectrum

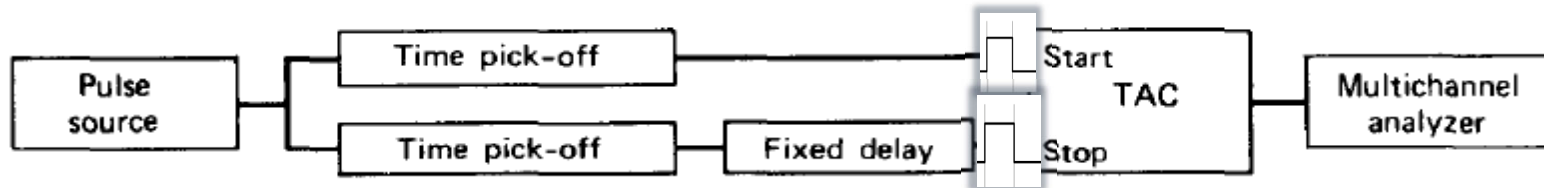
- The distribution of time intervals between start and stop pulses (= output pulses of TAC) can be recorded by a multichannel analyzer (= time spectrum)



Time spectrum

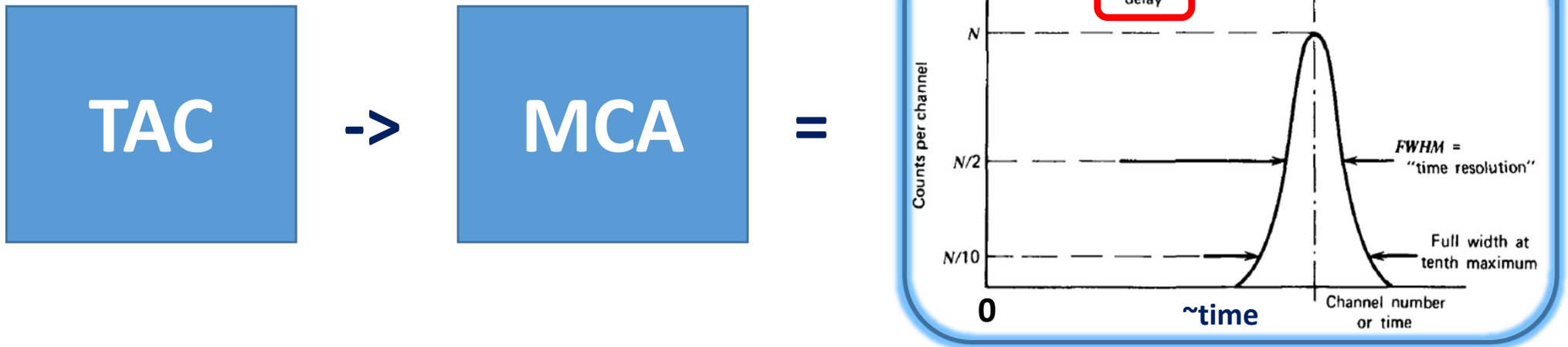

Short summary

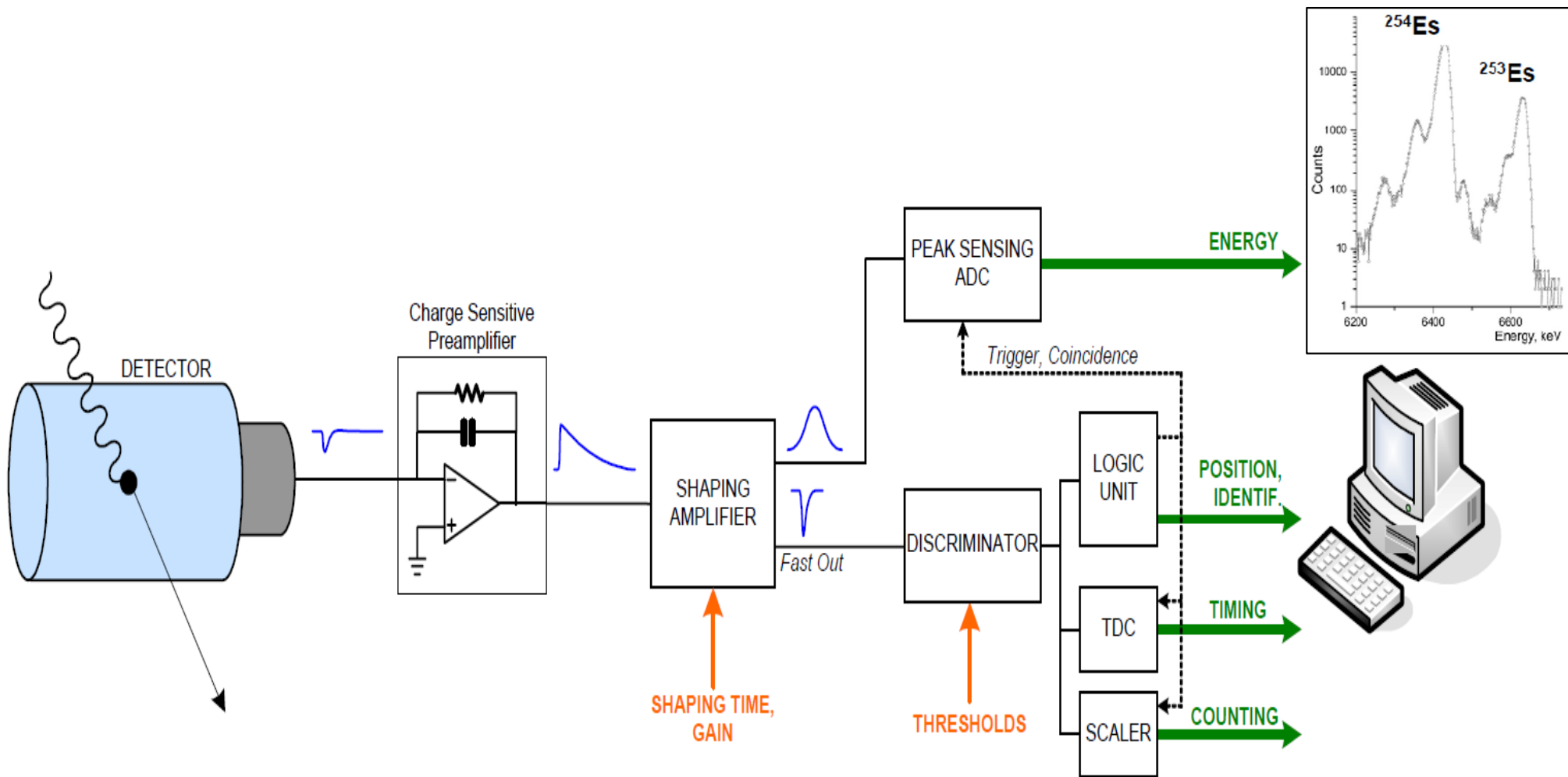

Pulse-processing: short summary of main players

Basic operation

- Preamplifier
- Linear/fast amplifier
- Discriminator (integral, differential(SCA))
- Time pick-off
- ...

“Assisting”..

- Splitter (fan-in/fan-out)
- Delay
- Pulse generator, ...

“Permission”...

- Linear gate
- Coincidence
- And/Or, ...

Result

- Counter
- TAC
- MCA/ADC
- ...



Information

(A) Linear-Linear	In	Out
PREAMPLIFIER	Linear charge pulse from the detector	Linear tail pulse
LINEAR AMPLIFIER	Linear tail pulse	Amplified and shaped linear pulse
BIASED AMPLIFIER	Shaped linear pulse	Linear pulse proportional to amplitude of input pulse that lies above input bias level
PULSE STRETCHER	Fast linear pulse	Conventional shaped linear pulse of amplitude equal to input pulse
SUM AMPLIFIER	Two or more shaped linear pulses	Shaped linear pulse with amplitude equal to the sum of coincident input pulses
DELAY	Fast linear or shaped linear pulse	Identical pulse after a fixed time delay
LINEAR GATE	(1) Shaped linear pulse (2) Gate pulse	Linear pulse identical to linear input if gate pulse is supplied in time overlap

(B) Linear-Logic	In	Out
INTEGRAL DISCRIMINATOR	Shaped linear pulse	Logic pulse if input amplitude exceeds discrimination level
DIFFERENTIAL DISCRIMINATOR (SINGLE-CHANNEL ANALYZER)	Shaped linear pulse	Logic pulse if input amplitude lies within acceptance window
TIME PICK-OFF (TRIGGER)	Fast linear or shaped linear pulse	Logic pulse synchronized with some feature of input pulse

(C) Logic-Linear	In	Out
START STOP	TIME-AMPLITUDE CONVERTER	Shaped linear pulse with amplitude proportional to Δt

(D) Logic-Logic	In	Out
COINCIDENCE	Logic pulses at two or more inputs	Logic pulse if pulses appear at all inputs within a time interval τ (resolving time)
ANTI-COINCIDENCE	Logic pulses at two inputs	Logic pulse only if pulse appears at one input <i>without</i> pulse at second input within time τ
SCALER	Logic pulses	One logic pulse for every N input pulses



PREAMP	Shaping amplifier	Pulse generator	Delay
Fast amplifier	Time pick-off (pulse appearance time)	Fan-in/ Fan-out	TAC
Linear Gate	Integral Discriminator	Coincidence	MCA
ADC	Counter	Timer	Count rate meter
Differential Discriminator (single channel analyser - SCA)	Timing + SCA	Anti-Coincidence	AND

Applications



Starting with a small problem...



Make a simple (very basic) scheme for a pulse counting

Starting with a small problem...

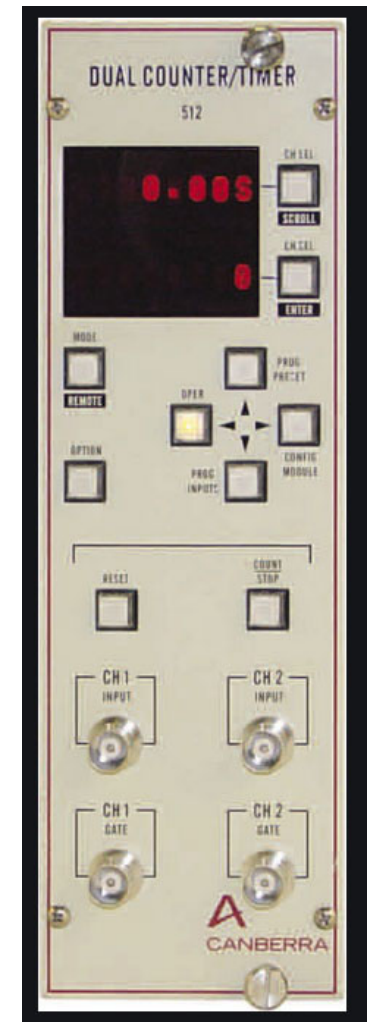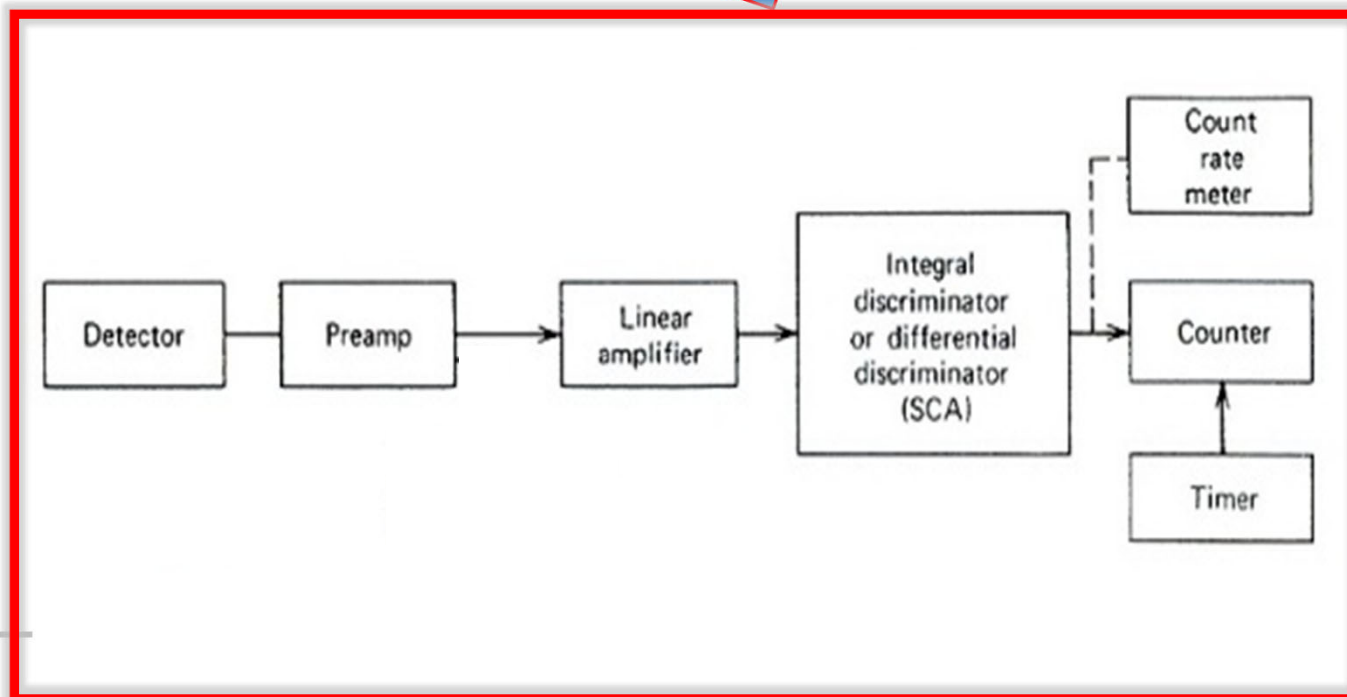Make a simple (very basic) scheme for a **pulse counting**




Another small problem...

Make a simple scheme to measure **energy spectrum**

Another small problem...

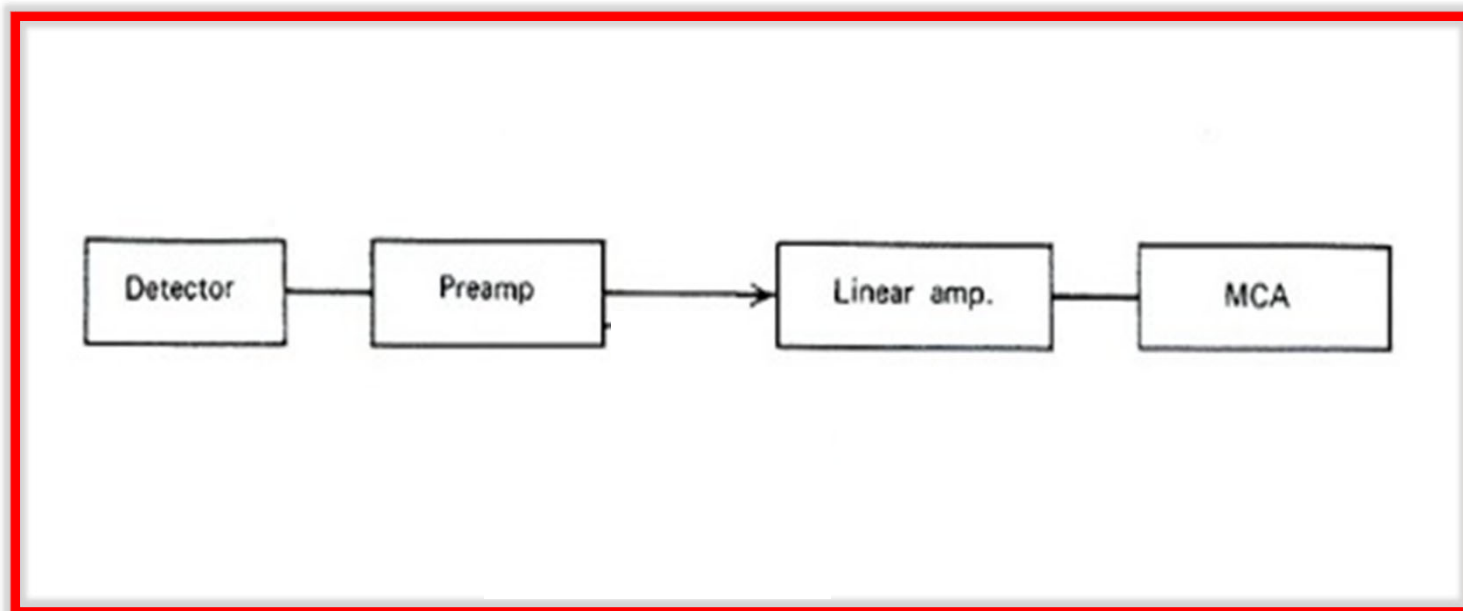Make a simple scheme to measure an **energy spectrum**





Approaching time measurements...



Make a simple scheme for recording multichannel
time spectra from a source emitting coincidence radiation


Towards time measurements...

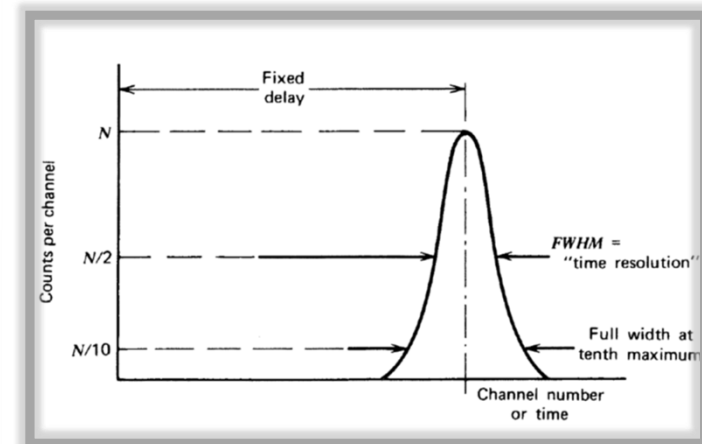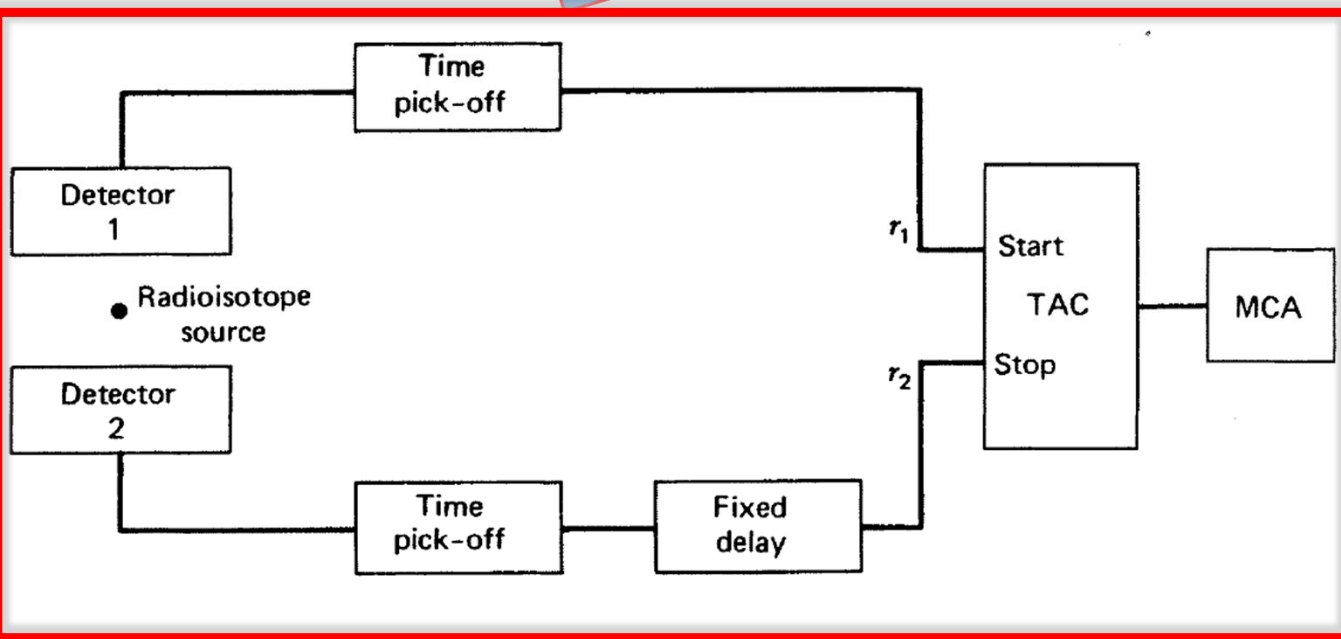Make a simple scheme for recording multichannel time spectra from a source emitting coincidence radiation



Explain the possible causes of constant background observed in a time spectrum when using a TAC.


Coincidence measurements...

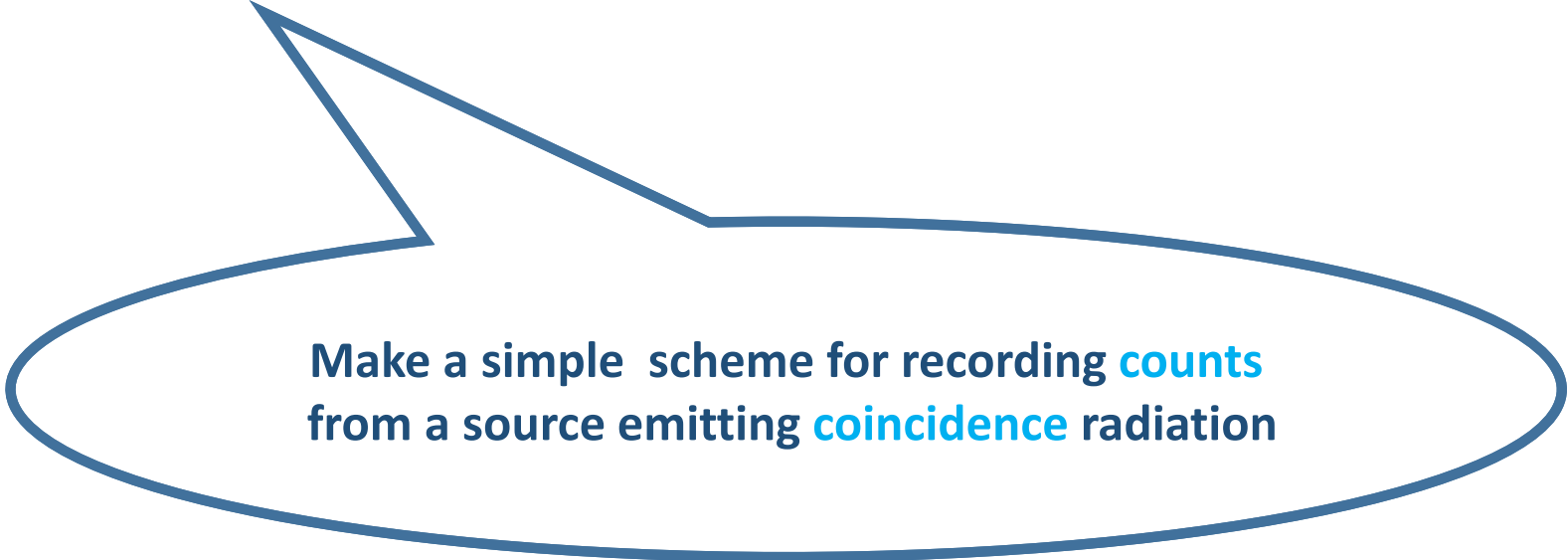

Make a simple scheme for recording **counts**
from a source emitting **coincidence** radiation

Coincidence measurements...

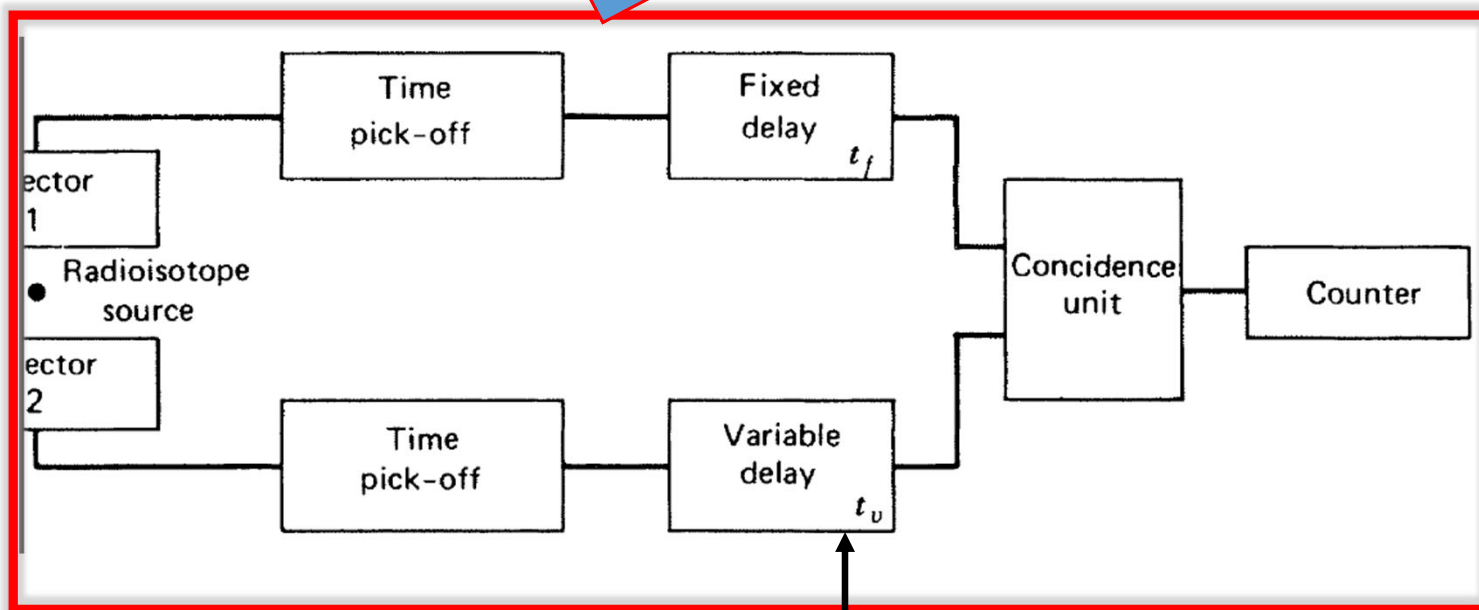Make a simple scheme for recording counts from a source emitting coincidence radiation




to make sure that two identical and simultaneous signals have spent the same time going through the electronics chain when they arrive at the TAC entrance

Counts "in time"

Coincidence measurements...

Make a simple scheme for recording counts from a source emitting coincidence radiation

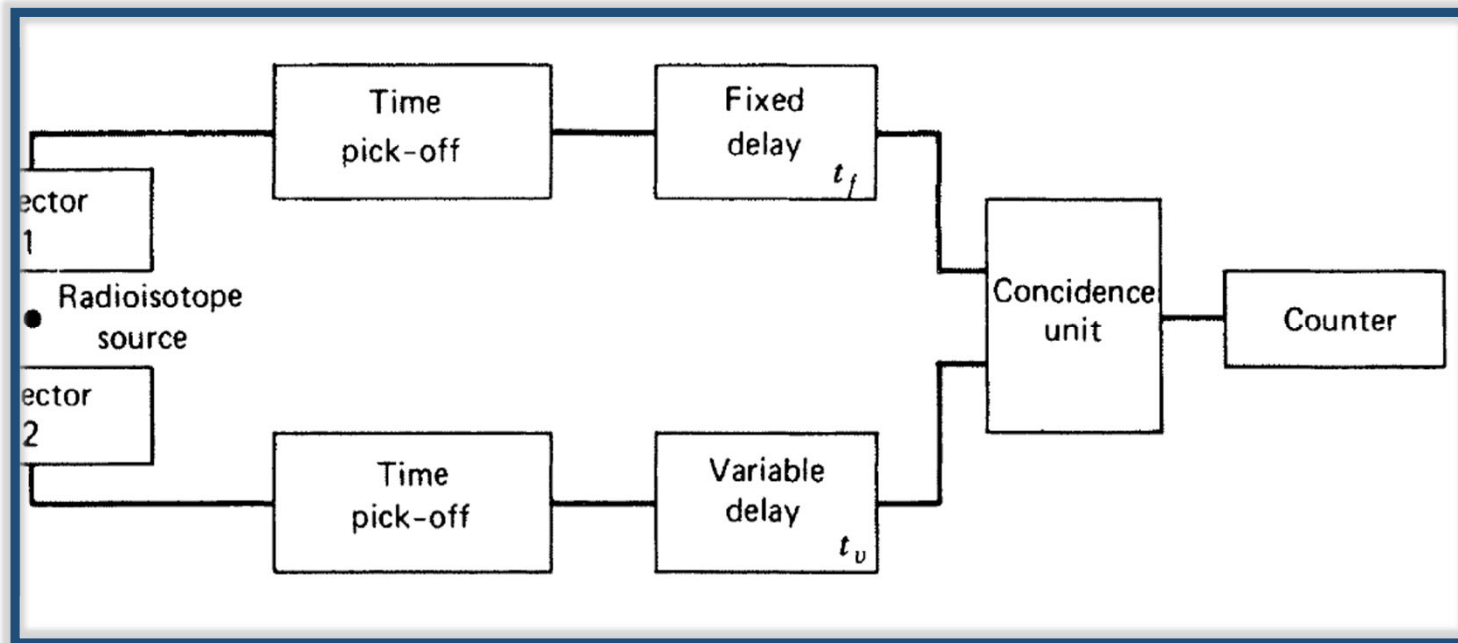...and MODIFY this for the case when pulse amplitude selection is desired




Counts "in time"

Coincidence measurements...

Make a simple scheme for recording counts from a source emitting coincidence radiation

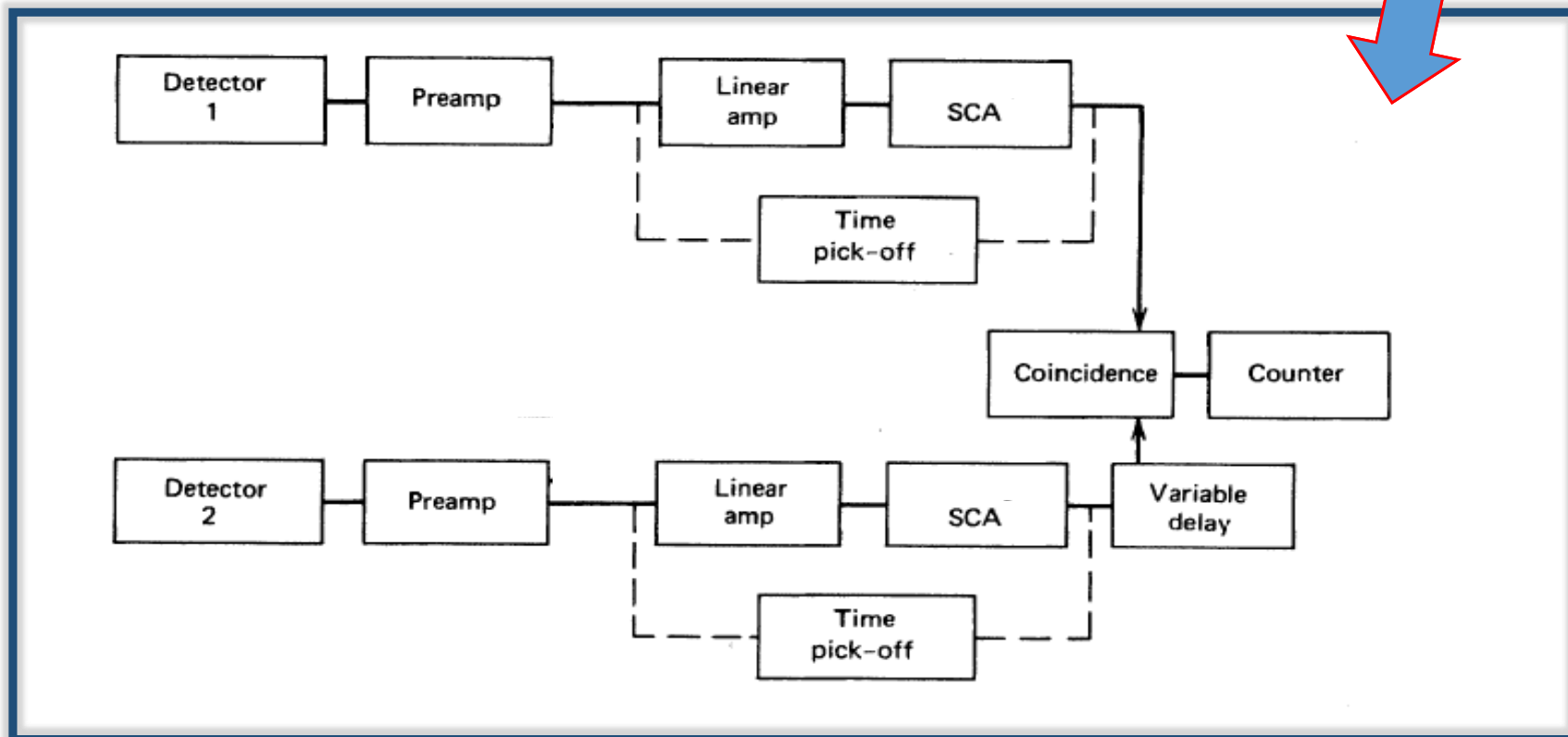...and MODIFY this for the case when pulse amplitude selection is desired




Counts "in time"

Coincidence measurements...

Make a simple scheme for recording counts from a source emitting coincidence radiation

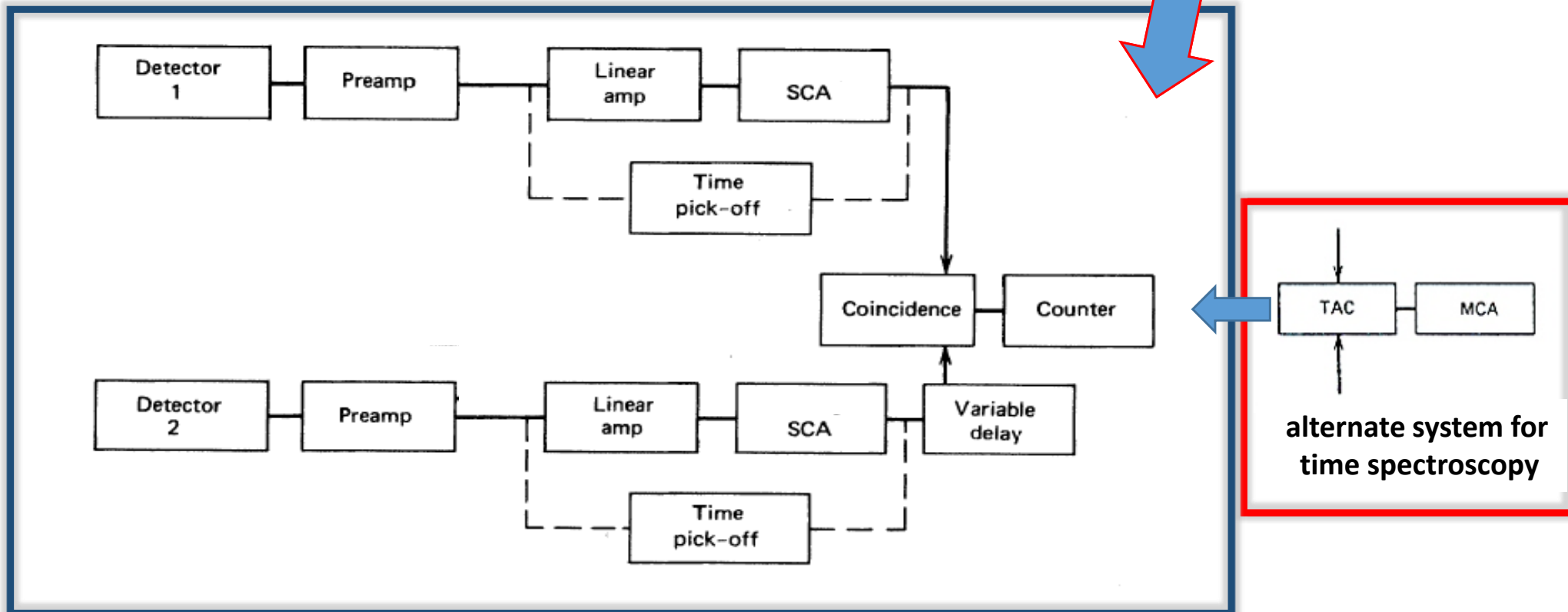...and MODIFY this for the case when pulse amplitude selection is desired




Counts "in time"

When **timing and amplitude** is important

Make a **fast-slow** pulse-processing system
in which a **slow amplitude branch** is used
to select only those **fast timing pulses**
that **correspond to events with certain amplitude**

When **timing and amplitude** is important

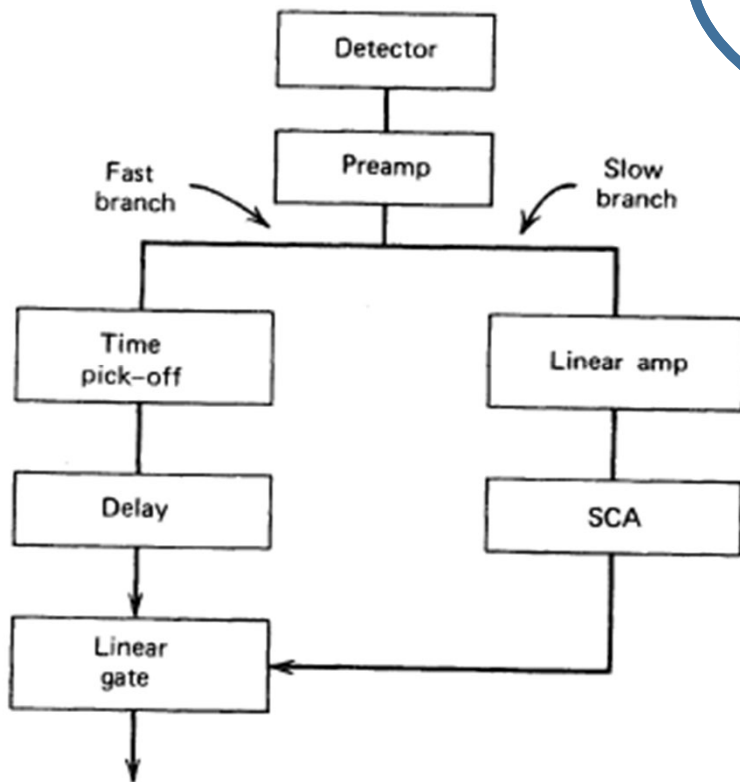Make a **fast-slow** pulse-processing system in which a **slow amplitude branch** is used to select only those **fast timing pulses** that correspond to events with certain amplitude



Anticoincidences

Propose a detector setup and electronic scheme for **suppression of the Compton edge** of a gamma spectrum **in a Ge detector**.

Anticoincidences

Propose detector setup and electronic scheme for **suppression of the Compton continuum** of a gamma spectrum in a Ge detector

