

# **ELECTRONICS - 2**

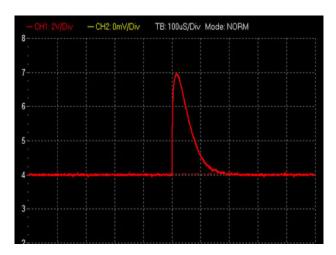


# General scheme

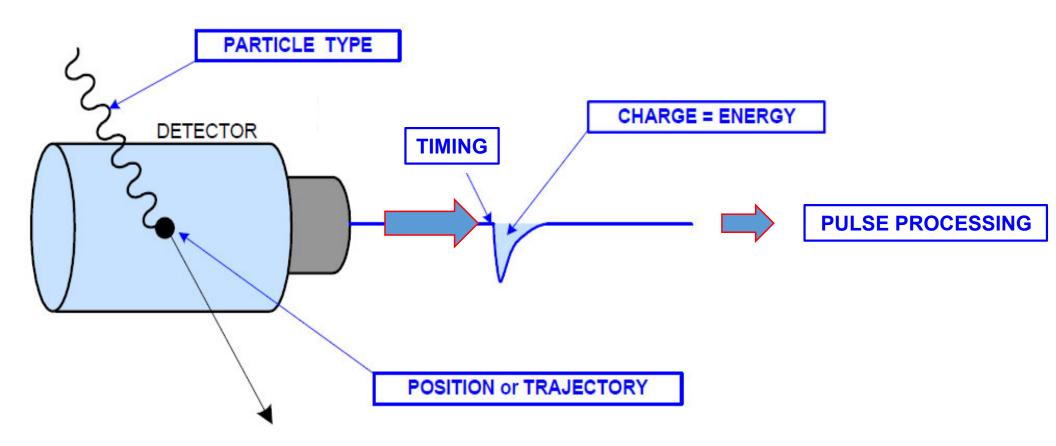

# Pulse: main actor


#### **PULSES:**

Linear: (analog)

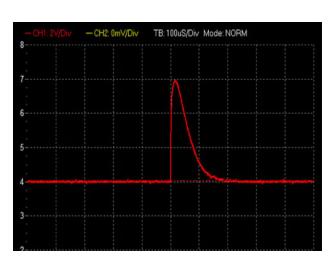


- Collection of output current by circuit;
   rise and fall generated by interaction
   of ionizing radiation with detector;
- the analysis of the amplitude of the pulse is the end result of a typical application;
- signal amplitude is proportional to the parameter of interest (e.g. the energy);

Logic: (digital)

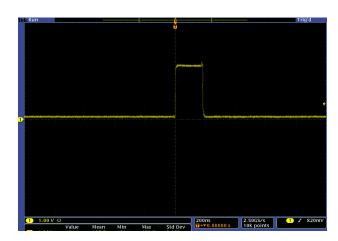


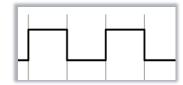- have a fixed shape and amplitude;
- convey information by their presence, absence, or relation to time (counts, timing).


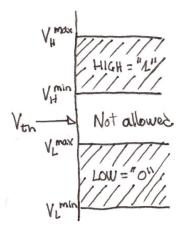
#### Standard digital pulses

 Digital signals encode information in a discrete number of states usually two



- $V_L^{min} < LOW < V_L^{max}$
- $V_H^{min} < HIGH < V_H^{max}$
- The values in the range  $[V_L^{max}, V_H^{min}]$  are undefined.
- $V_{th}$  is the typical logic threshold between '0' and '1'.

LPHYS2102

#### Standard digital pulses


		V <sub>cc</sub>	$V_L^{min}$	$V_L^{typ}$	$V_L^{max}$	$V_{th}$	$V_H^{min}$	$V_H^{typ}$	$V_H^{max}$
TTL	inp	+5V	-0.4V		+0.8V	+1.2 V	+2.0V		+5.4V
	out		+0.0V	+0.2V	+0.4V		+2.4V	+3.3V	+5.0V
CMOS	inp	+5V	-0.2V		+1.5V	+2.5 V	+3.3V		+5.4V
	out		+0.0V	+0.2V	+0.4V		+4.6V	+4.9V	+5.0V
ECL	inp	-5.2V	-5.0V		-1.5V	-1.3V	-1.1V		-0.0V
	out		-1.9V	-1.8V	-1.6V		-1.0V	-0.9V	-0.8V
NIM	inp	±12V	-2.0V		+1.5V		+3.0V		+12.0V
(slow)	out	±24V	-2.0V	+0.0V	+1.0V		+4.0V	+6.0V	+12.0V
NIM	inp	±12V	-4.0mA		+20mA		-12mA		-36mA
(fast)	out	$\pm 24V$	-1.0mA	+0.0 mA	+1mA		-14mA		-18mA

- ullet NIM: Mechanical and electrical standard for nuclear instrumentation. Levels defined in terms of currents. Logic 1 = 16 mA
- TTL: Widely electrical standard. Levels defined only in terms of voltage
- ECL: Differential electrical standard

→□▶→□▶→□▶→□▶ □ 900

# **Pulse-processing instruments: NIM**
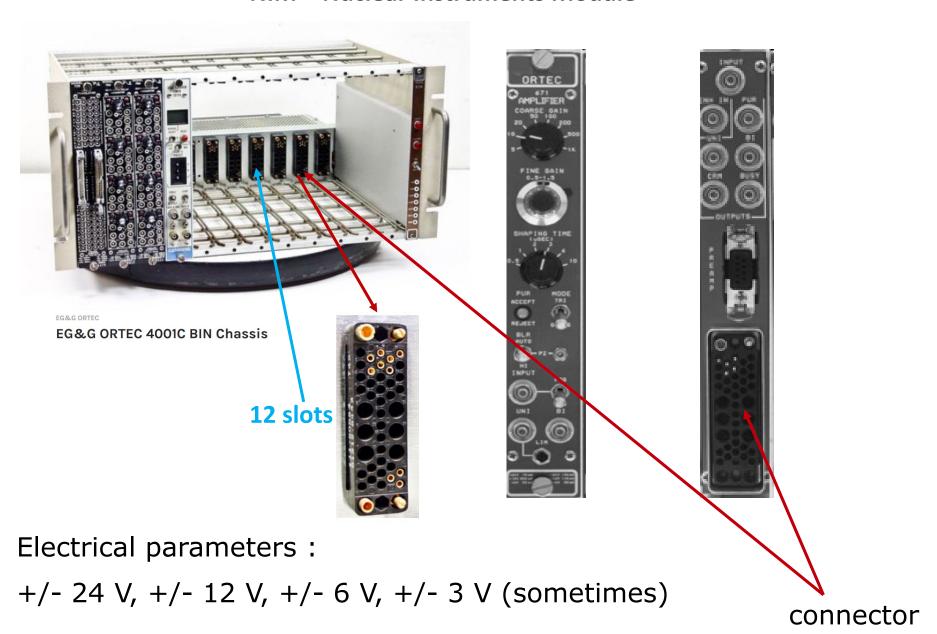
#### **NIM** = Nuclear Instruments Module



## **Pulse-processing instruments: CAMAC**

#### CAMAC = Computer Automated Measurement and Control

Main difference with NIM – computer interface





Controller serves as interface between the modules in the bin Back plane contains power bus as well as data bus Slots 24 & 25 reserved for the controller

# Pulse-processing instruments: examples of CAMAC modules







LeCroy 2280 ADC System Processor CAMAC Module

**LeCroy CAMAC Modules** 

## Pulse-processing instruments: VME

VME = Versa Module Eurocard (Europa)



Developed in 1981 by Motorola

Much more compact, high speed bus

Fiber optic communication possible

## Pulse-processing instruments: example of VME-board

#### VME – Versa Module Eurocard (Europa)



**V976** 


Quad 4 Fold AND/OR/MAJ, NIM-TTL TTL-NIM Translator, Fan-In Fan-Out

- Four independent sections with four channels each
- TTL and NIM inputs automatically detected
- NIM/TTL selectable output level
- AND, OR, Majority function with selectable number of inputs
- Logic Fan In / Fan Out
- Selectable direct or negated output



## Pulse-processing instruments: example of VME-board
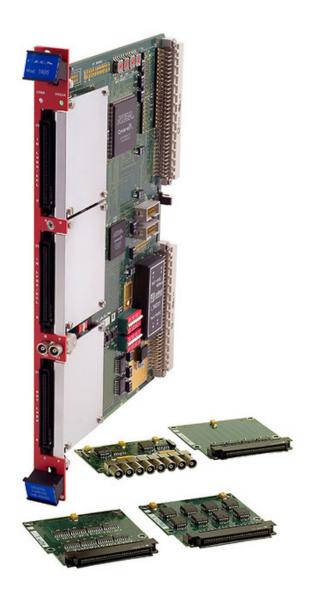
#### VME – Versa Module Eurocard (Europa)



## V1495

#### **General Purpose VME Board**

- User customisable FPGA Unit (with preloaded demo code)
- LVDS/ECL/PECL inputs (differential)
- 64 inputs, expandable to 162 (with 32 outputs)
- 32 outputs, expandable to 130 (with 64 inputs)
- 405 MHz maximum frequency supported by clock tree for registered logic
- I/O delay smaller than 15 ns (in Buffer Mode)
- Programmable 3-color LED
- Libraries (C and LabView) and Software tools for Windows and Linux



# **Pulse-processing units**


properties and intro to modules

# Pulse-processing units: "crude" role classification


#### **Basic operation**

- > Preamplifier
- ➤ Linear/fast amplifier
- ➤ Discriminator
- ➤ Time pick-off
- > etc

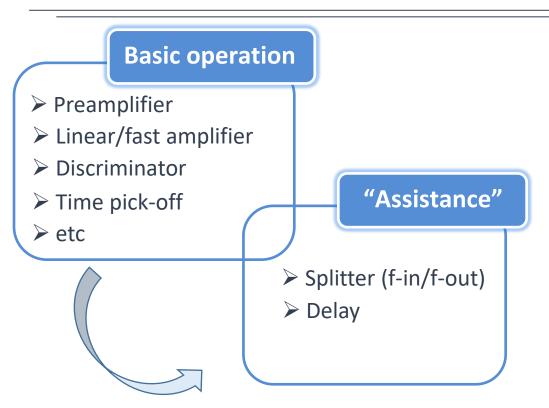
# Pulse-processing units: "rude" role classification


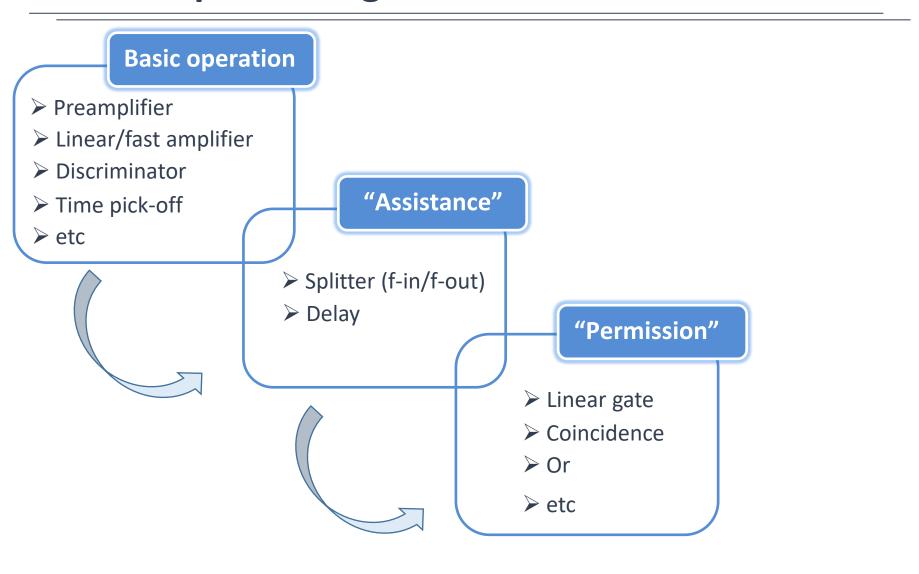
# Pulse-processing units: "rude" role classification


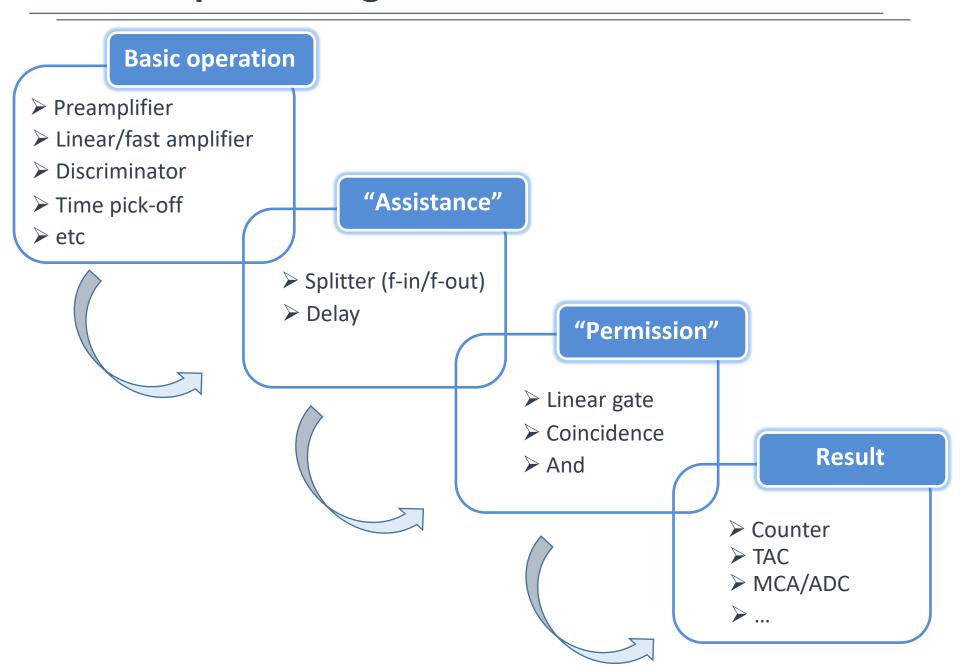
# Pulse-processing units: "rude" role classification





# Pulse-processing units: "crude" role classification

#### **Basic operation**

- > Preamplifier
- ➤ Linear/fast amplifier
- ➤ Discriminator
- ➤ Time pick-off
- > etc

## **Preamplifier**

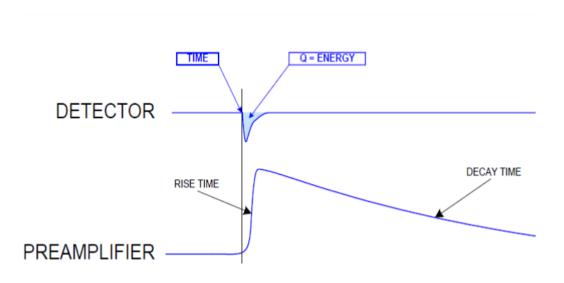

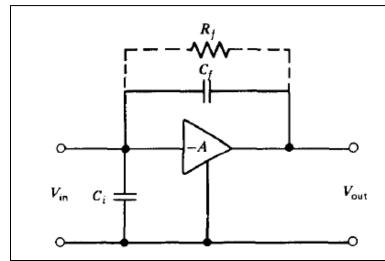

**Input:** linear charge pulse from detector

**Output:** linear tail pulse with amplitude proportional to input

Rise time: as short as possible (consistent with charge collection time)

Decay time: long(~50-100μs)

Output amplitude:  $V_{out} = \frac{Q}{C} \approx 10s-100s \text{ mV}$ 

# **Basic operation**






**Model 2003BT Silicon Detector Preamplifier** 



## Linear (shaping) amplifier

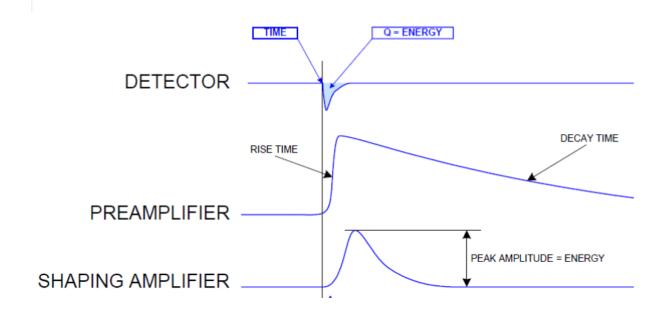

**Input:** linear tail pulse from preamplifier

**Output:** amplified and shaped linear pulse

**Shaping time :**  $\sim$ 0.5-10 $\mu$ s

**Output amplitude:** V<sub>out</sub> ≈ 0-10 V

## **Basic operation**






#### 572A Amplifier

- General-purpose amplifier for energy spectroscopy with all types of detectors
- Built-in pile-up rejector and gated BLR with automatic thresholds for excellent performance at high counting rates
- Unipolar and bipolar outputs
- Active filter networks with wide range of time constants
- Wide gain range



# **Fast amplifier**

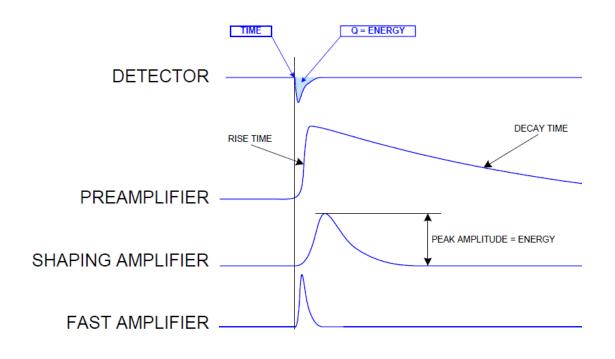


**Input:** linear tail pulse from preamplifier

**Output:** fast (short length) linear pulse

**Timing:** few ns


Output amplitude: V<sub>out</sub> ≈ few V

## **Basic operation**

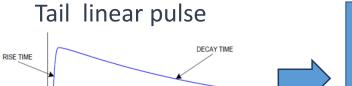

# Fast amplifier



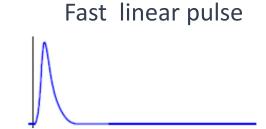



#### 9309-4 Quad Fast Amplifier

- Rise Time <1.5-ns (for unipolar ≤±25 mV inputs).</li>
- DC Coupled to allow high counting rates.
- 0 to 10 Adjustable Gain to provide flexible gain requirements.
- Two Outputs for each Amplifier allows simultaneous counting and timing.



## **Discriminator**

#### **❖** Integral disciminator

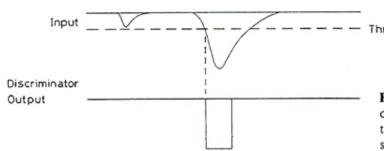



Fig. 14.14. Discriminator operation: only signals whose amplitude is greater than the fixed threshold trigger an output signal

**Input:** shaped linear pulse

Output: logic pulse if input amplitude exceeds discrimination level D

#### **Discriminator**

#### Integral disciminator

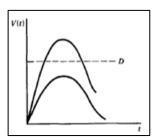


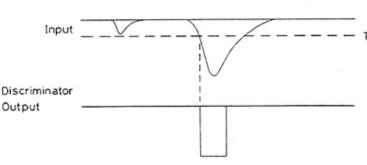



Fig. 14.14. Discriminator operation: only signals whose amplitude is greater than the fixed threshold trigger an output signal

Input: shaped linear pulse

**Output:** logic pulse if input amplitude exceeds discrimination level
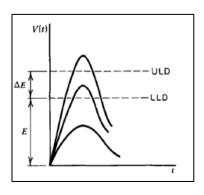
#### Differential discriminator (Single Channel analyzer)



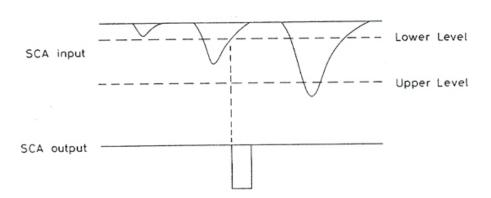

<u>Input:</u> shaped linear pulse

**Output:** logic pulse if input amplitude lies within acceptance window


#### SCA: Single channel Analyzer


- In a large number of applications we are interested in counting the number of interesting events
  - Interesting: pulses generated by radiation passage pulses lying in an energy band
- Rest of pulses should be "cleaned-up"

- This step is necessary in almost all readout chain to eliminate
  - unavoidable existence of noise
  - spurious pulses

LPHYS2102

#### SCA: Technical Implementation

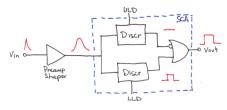

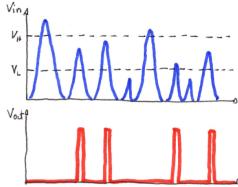

## **Basic operation**


Shaped linear pulse






Logic pulse



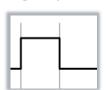




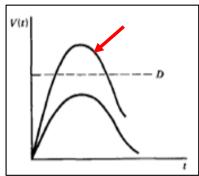Logic pulse at output for every input pulse with amplitude above threshold level D




e.g. ORTEC 850 Quad **Single Channel Analyzer** (Differential Discriminator)

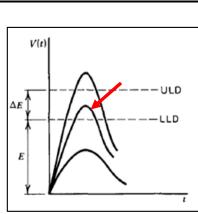Logic pulse at output for every input pulse with amplitude between the upper threshold level ULD and the lower threshold LLD





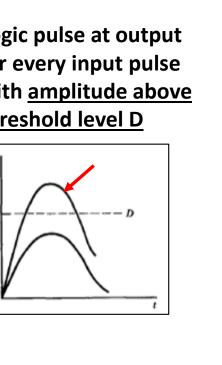

#### **Timing Information**

- Timing refers to the determination of the time arrival of a pulse
- Timing information is used to:
  - Control the time evolution of a process
  - Measurement of coincident events (trigger, cleaning, ...)
  - ► Time of flight techniques (particle id, trigger, ....)

- Many methods developed but all of them based in measure the time on a certain point of the signal development
  - Leading-Edge Timing Method
  - Zero-Crossing Timing Method
  - Constant Fraction Timing Method




## Time pick-off (trigger)
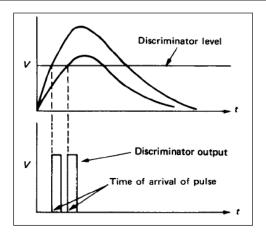
## Leading edge timing

Records the time when the pulse crosses a fixed discrimination level for amplitude.

Used for pulses with similar shape and amplitude.



#### Leading-Edge Timing Method

- Time determination with the help of a discriminator
  - Time measured with the output signal of the discriminator
  - Usually used the leading edge.
  - Trailing edge can be affected of stray capacitances, etc...
- Heavily affected by walk and jitter
  - Walk time: Time difference induced by different rise-time slope from different pulses
  - Jitter: electronic noise

Walk time can be sometimes corrected with Time-Over-Threshold


- Threshold level is critical
  - ▶ Low thresholds may allow to pass a fraction of random noise
  - ▶ Large thresholds may reduce the number of valid thresholds

## Time pick-off (trigger)
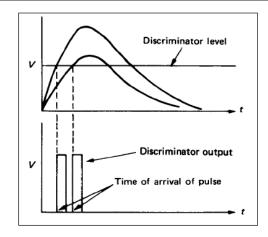
## Leading edge timing

Records the time when the pulse crosses a fixed discrimination level for amplitude.


Used for pulses with similar shape and amplitude.


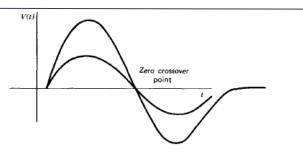
#### Zero Cross-over timing


Records the time at which the <u>waveform crosses from</u> the positive to the negative side (requires bipolar shape).

Used for pulses with <u>large variation in **amplitude**</u>.



#### Zero-crossing method

- Effects due to jitter and walk time ca be avoided using the time from the zero crossing of a bipolar pulse
  - Based on the fact that the zero-crossing point is "independent" of pulse height
  - Jitter is reduced but not eliminated
  - Small walk dependence depending on risetime
- Needed to generate a bipolar pulse: problems with high rates

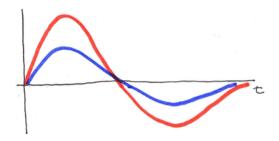


June 2021

## Time pick-off (trigger)
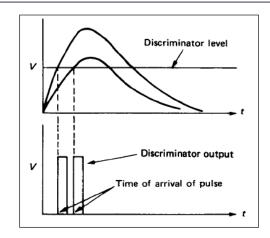
## Leading edge timing

Records the time when the pulse crosses a fixed discrimination level for amplitude.


Used for pulses with similar shape and amplitude.


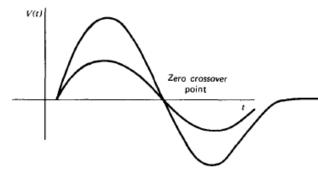
#### Zero Cross-over timing

Records the time at which the <u>waveform crosses from</u> the positive to the negative side (requires bipolar shape).


Used for pulses with <u>large variation in **amplitude**</u>.


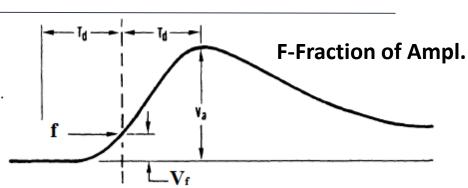
#### Constant fraction timing

Records the <u>time after which the leading edge</u> of the pulse <u>has reached a *constant fraction*</u> of the peak pulse amplitude.


Used for <u>pulses with similar **shape**</u>, independent of the amplitude.



#### Constant-Fraction Method

- Most efficient and versatile timing method
- Timing signal is generated at a constant fraction (k) of its pulse height o walk time free
- Technique based on empirical test showing that there is an optimal threshold for timing. Depends on each signal
  - 1. Input signal is split in two
  - 2. One signal is inverted and attenuated by the fraction k
  - 3. The other signal is delayed by the time au it takes to arrive to this fraction
  - 4. Both signals are summed and the zero-crossing point of the resulting signal is used
- This technique uses zero-crossing, but unlike this, a bipolar pulse is not required.
- Timing method needed when high time resolutions are required (< 100ps)

#### Constant-Fraction Method

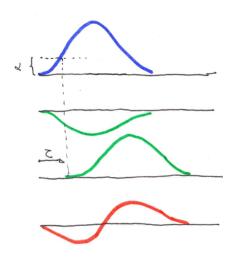

$$f(t) = \sqrt{(t-2)} - \sqrt{\sqrt{(t)}} = 0$$

$$\sqrt{(t-2)} = \sqrt{\sqrt{(t-2)}}$$

$$\sqrt{(t-2)} = \sqrt{\sqrt{(t-2)}}$$

$$\sqrt{(t-2)} = \sqrt{\sqrt{(t-2)}}$$


$$\sqrt{(t-2)} = \sqrt{\sqrt{(t-2)}}$$

#### Time pick-off (trigger)
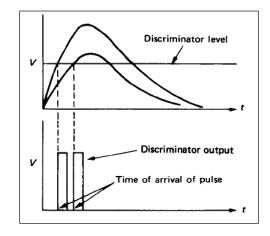
#### Leading edge timing

Records the time that the pulse crosses a fixed discrimination level for amplitude.


Used for pulses with similar shape and amplitude.


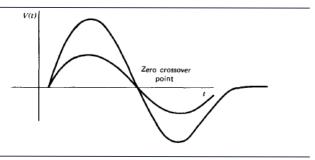
#### Zero Cross-over timing

Records the time at which the waveform crosses from the positive to the negative side (requires bipolar shape).


Used for pulses with large variation in amplitude.


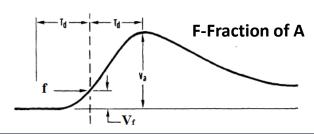
#### Constant fraction timing

Records the time after the leading edge of the pulse has reached a *constant fraction* of the peak pulse amplitude.

Used for pulses with similar shape, independent of the amplitude.



**Input:** fast linear or shaped linear pulse

Output: logic pulse synchronized with some feature of input pulse

#### **Basic operation**

Fast (shaped)
linear pulse



# Time pick-off

(pulse appearance time)



Logic pulse



#### **Features**


- Four CF discriminators in a single-width NIM
- 200 MHz count rate capability
- 1000:1 dynamic range
- Typical walk <±30 ps for 100:1 dynamic range
- Selectable fraction or leading edge operation
- Output indicator LEDs
- Gated operation



Model 454 200 MHz Quad Constant Fraction Discriminator


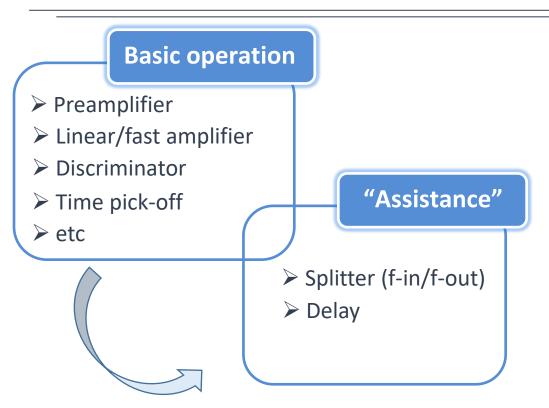
## Pulse-processing units: "rude" role classification



# "Assisting"

#### Shaped linear pulse





# Fan-in/ Fan-out







Two identical pulses






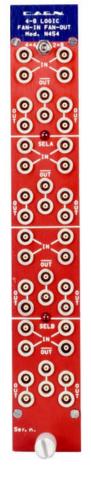4-8 Logic FAN-IN/FAN-OUT

- 4 independent sections with 4 inputs each
- OR output with fan out of four per section
- Possibility of cascading channels to form dual 8-fold fan-in/fan-out
- Input/output delay less than 7 ns
- 100 MHz max. input frequency





#### "Assisting"

# **DELAY**

Signal ~66% of light speed (5ns/m)



Input: linear pulse (fast or shaped)

**Output:** identical pulse after fixed time delay

## "Assisting"

To <u>test electronics</u> and <u>monitor dead time</u>

# Pulse generator




Exponential linear pulse (you set frequency and amplitude)



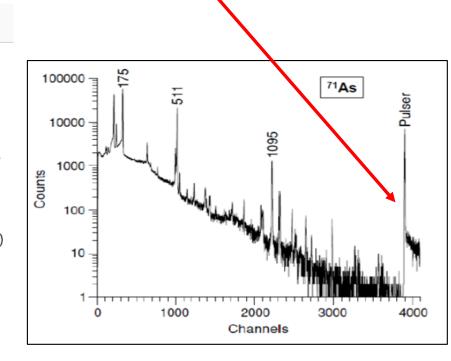
#### 419 Precision Pulse Generator

- Simulates detector output signals
- Precision dial may be calibrated to read directly in terms of equivalent energy deposition in semiconductor radiation detectors
- Exponential pulse shape with 5- to 250-ns rise time and 200- or 400-µs decay time constant
- Line frequency or 70-Hz pulse rate
- Positive or negative polarity
- Direct 0 to 1-V output (0 to 10 V with external reference voltage)
- Attenuated output with 2000:1 attenuation range
- Internal or external reference voltage





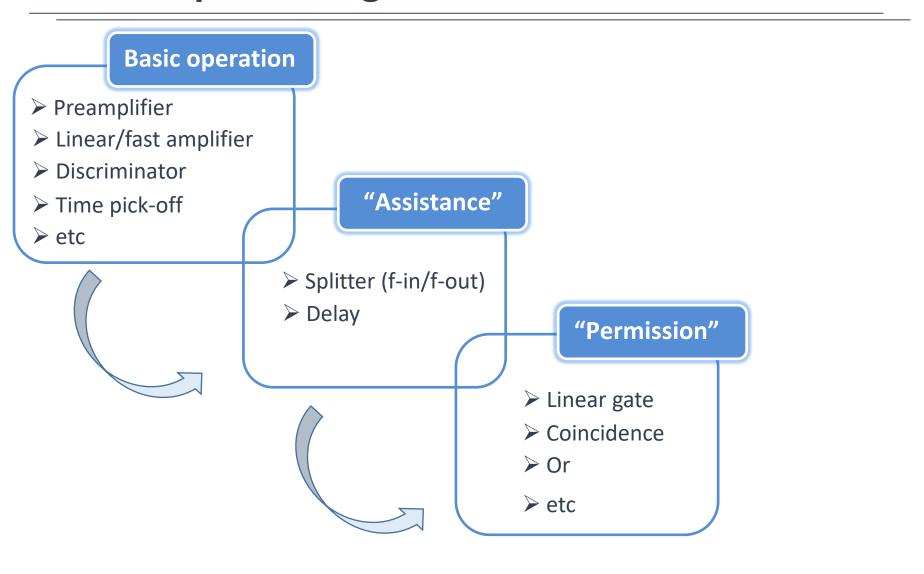
## Pulse-processing units: "rude" role classification


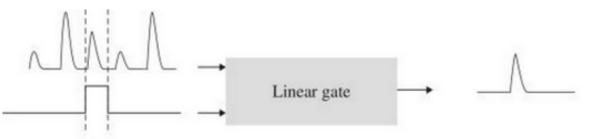
#### "Permission" units: linear gate

❖ Linear gate **permits** a signal when it is accompanied with a logic pulse




Input: 1) shaped linear pulse and 2) gate pulse (logic)


Output: linear pulse identical to input if gate (logic) pulse is supplied in time overlap
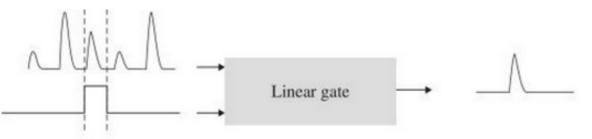
#### "Permission" unites: linear gate

❖ Linear gate **permits** a signal when its accompanied with a logic pulse



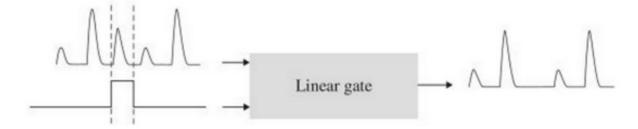❖ Linear gate **blocks** a signal when its accompanied with a logic pulse



**Input:** 1) shaped linear pulse 2)gate pulse

Output: linear pulse identical to input if gate (logic)pulse is supplied in time overlap


#### "Permission"

Shaped linear pulse







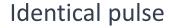







#### 426 Linear Gate

- For passing and blocking analog signals in the range from +0.2 to +10 V
- Ungated or gated with coincidence or anticoincidence gating
- External or internal control of gate pulse width

The ORTEC Model 426 Linear Gate provides a variable gate duration with width controlled by a single-turn front-panel-mounted potentiometer.



### "Permission-Assisting"

Shaped linear pulse






Gate-and-Delay Generator



Shaped linear pulse





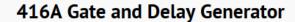


- Provides <u>adjustment of the delay, width, polarity, and amplitude of gating</u> pulses
- Positive or negative polarity input pulse
- Time delay from 0.1 to 110 µs
- Output pulse width from 0.4 to 4 µs
- · Excellent time delay stability





#### "Permission" units: coincidences

Coincidence(anticoincidence)

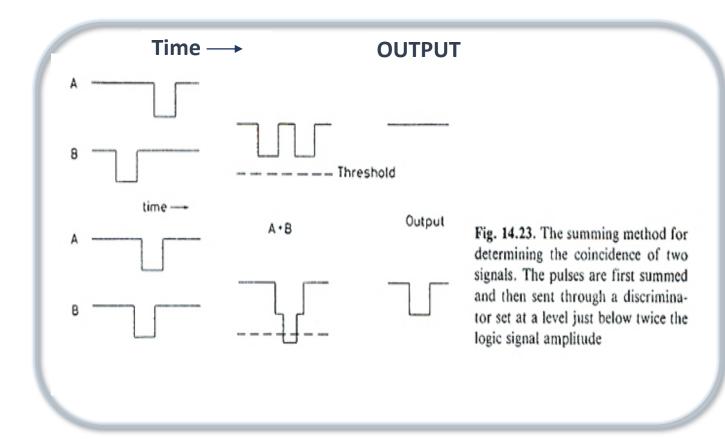

**Input:** logic pulses (for timing!) at two or more inputs

**Output:** logic pulse if pulses appear at all inputs at time interval  $\tau$  (resolving time)

#### "Permission"


2 Logic pulses



Coincidence (anti)



Logic pulse

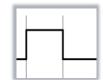



#### N455

**Quad Coincidence Logic Unit** 

- 4 identical independent sections
- Two inputs per section
- 130 MHz Max input frequency
- 6 ns double pulse resolution
- 10 ns I/O delay
- Switch selectable AND/OR logical function
- Adjustable output FWHM (4 to 650 ns)
- Overlap output
- Common Veto

